

R18

Code No: 153AB

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year I Semester Examinations, October - 2020

ANALOG AND DIGITAL ELECTRONICS

(Common to CSE, IT)

Time: 2 hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- 1.a) Define Diffusion capacitance? Also derive the expression for C_D ?
b) Draw and explain the V-I characteristics of a tunnel diode? [8+7]
- 2.a) What is LED? Explain the construction of LED in brief?
b) Explain the working of a full wave rectifier with necessary waveforms? [7+8]
- 3.a) Explain the input and output characteristics of common base configuration.
b) Explain thermal run away and thermal stability. [8+7]
4. Analyse CE-CE amplifier in terms of gains and Impedances. [15]
- 5.a) Draw and explain the CS amplifier with current source load.
b) Explain the small signal MOSFET circuit model. [8+7]
- 6.a) Explain ECL gate and write the advantages and disadvantages.
b) Draw CMOS NOT gate and then explain the same. [8+7]
7. Simplify the following Boolean function using Quine – McClusky method.
 $F(A, B, C, D) = \sum m (0, 2, 3, 6, 7, 8, 10, 12, 13)$ [15]
- 8.a) What is state assignment? Explain with a suitable example?
b) Realize D and T flip flops using Jk flip flops. [8+7]

---ooOoo---