

R15

Code No: 123CT

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year I Semester Examinations, November/December - 2016

DIGITAL LOGIC DESIGN

(Computer Science and Engineering)

Time: 3 Hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART-A

(25 Marks)

- 1.a) Explain duality theorem with example. [2]
- b) Convert following hexadecimal number to decimal.  
i)  $F28_{16}$  ii)  $BC2_{16}$ . [3]
- c) Implement EX-NOR gate using only NAND gates. [2]
- d) Obtain the prime implicants for given Boolean expression using K-map.  
 $f(A, B, C) = \sum(1, 3, 6, 7)$ . [3]
- e) What is code converter? [2]
- f) Explain the analysis procedure for combinational circuit. [3]
- g) Explain clear and preset inputs. [2]
- h) What is race around condition? [3]
- i) Explain the role of Cache Memory in sequential circuits. [2]
- j) Compare ROM and RAM. [3]

PART-B

(50 Marks)

- 2.a) Using 2's complement perform  $(42)_{10} - (68)_{10}$ . [2]
  - b) Implement the following Boolean function with NOR-NOR logic  
 $F(A, B, C) = \pi M(0, 2, 4, 5, 6)$ . [5+5]
- OR
- 3.a) What is the specialty of unit-distance code? State where they are used.
  - b) Give the Boolean expressions used for following gates  
i) AND ii) NOR iii) EX-OR iv) OR v) EX-NOR. [5+5]
4. Reduce the following functions using K-map techniques.
- a)  $f(A, B, C, D, E) = \sum m(1, 4, 8, 10, 11, 20, 22, 24, 25, 26) + d(0, 12, 16, 17)$
  - b)  $f(A, B, C, D) = \pi M(4, 5, 6, 7, 8, 12, 13) + d(1, 15)$ . [5+5]
- OR
- 5.a) Using K-map obtain the minimal sum of products and the minimal product of sums from of the function  $f(a, b, c, d) = \sum m(1, 2, 3, 5, 6, 7, 8, 13)$ .
  - b) Explain about essential prime implicants. [5+5]
6. Design the full adder circuit using decoder and de-multiplexer. [10]
- OR
- 7.a) Write a short note on priority encoder.
  - b) What is decoder? [5+5]

01 01 01 01 01 01 01

8.a) Compare combinational circuits and sequential circuits. [5+5]  
b) Explain the clocked JK flip-flop with truth table. [5+5]

OR

9. Draw and explain the working of following flip-flops:  
a) RS b) D. [5+5]

10.a) Draw and explain the block diagram of PLA. [5+5]  
b) Explain address and data bus in digital electronics. [5+5]

OR

11. Implement the following function using a PROM. [5+5]  
a)  $F(A, B, C, D) = \sum m(1, 9, 12, 15)$   
b)  $G(A, B, C, D) = \sum m(0, 1, 2, 3, 4, 5, 7, 8, 10, 11, 12, 13, 14, 15)$

---0000---

01 01 01 01 01 01 01

01 01 01 01 01 01 01

01 01 01 01 01 01 01

01 01 01 01 01 01 01

01 01 01 01 01 01 01

01 01 01 01 01 01 01