

Code No: 114AF

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**B.Tech II Year II Semester Examinations, May-2015****DIGITAL DESIGN USING VERILOG HDL****(Electronics and Communication Engineering)**

Time: 3 Hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART- A**(25 Marks)**

- 1.a) Write difference between tasks and functions. [2M]
- b) Illustrate with an example Array of Instances of Primitives. [3M]
- c) What are Tristate gates? [2M]
- d) Mention data types used in Verilog HDL. [3M]
- e) Write any two sequential models can be used. [2M]
- f) Write about bidirectional gates. [3M]
- g) What are parallel blocks? [2M]
- h) What are time delays with switch primitives? [3M]
- i) Draw the diagram of NAND gate using CMOS switches. [2M]
- j) Write Verilog code using Case statement. [3M]

PART-B**(50 Marks)**

2. Explain the following "lexical conventions" with examples. [3+3+4]
a) White space b) strengths c) Operators

OR

- 3.a) Write a short notes on concurrency and functional verification. [5+5]
- b) Explain port Declaration with an example using Verilog code.

- 4.a) Classify and explain strengths and contention resolution.
- b) Write Verilog code for 1 to 4 demultiplexer module by using 2 to 4 decoder? [5+5]

OR

- 5.a) Write Verilog module for a positive edge triggered flip flop with test bench. [5+5]
- b) Explain how the ALWAYS statements are used in Verilog.

- 6.a) Design Verilog module Event construct for a serial data receive and test bench for the same. [5+5]
- b) Design a counter module and test bench to illustrate the use of WAIT.

OR

- 7.a) Describe procedural continuous assignment statements assign, de assign, force and release.
b) Explain the compiles directives in detail. [5+5]
- 8.a) Design CMOS switch of parallel combination.
b) Explain and specify blocks of Path Delay Modeling. [5+5]
- OR**
- 9.a) Write the code for CMOS switch of parallel combination.
b) Briefly explain combinational and sequential UDPs in Verilog. [5+5]
- 10.a) Write the verilog code for basic functional unit of a dynamic shift register.
b) Write a short note on Design verification. [5+5]
- OR**
- 11.a) Briefly explain any one method used for sequential circuit testing.
b) Write Verilog module for 8-bit comparator with test bench. [5+5]

---00000---