

**R18**

Code No: 153AN

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**

**B. Tech II Year I Semester Examinations, December - 2019**

**DIGITAL SYSTEM DESIGN**

**(Electronics and Communication Engineering)**

**Time: 3 Hours**

**Max. Marks: 75**

**Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A. Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b as sub questions.

**PART-A**

**(25 Marks)**

- 1.a) Given that  $(292)_{10} = (1204)_b$ , Determine b. [2]
- b) Write a note on 'display decoders'. [2]
- c) What is the difference between Latch and Flip Flop? [2]
- d) What is Moore and Mealey machine? [2]
- e) Draw the circuit for CMOS AND-OR Invert (AOI) logic gate. [2]
- f) Add (98) and (89) in Excess-3 form. [3]
- g) Realize the function  $f_1 = A \oplus B \oplus C$  using two half adders: Use additional gates if necessary. [3]
- h) Differentiate combinational and sequential circuits. [3]
- i) List the limitations of finite – state machines. [3]
- j) What are the precautions to be taken while handling CMOS logic gates? [3]

**PART-B**

**(50 Marks)**

- 2.a) Find the complement of the Boolean function  $(AB'+CD')(B'C+A'D)$  and reduce it to a minimum number of literals.
- b) Determine the Canonical sum-of-products form for  $T(x,y,z)=x'y+z'+xyz$ . [5+5]

**OR**

- 3.a) Show the weights of three different four bit Self-Complementing codes whose only negative weight is -4.
- b) Convert the function  $f(x,y,z) = \pi(0,3,6,7)$  to the other canonical form. [5+5]

- 4.a) Minimise the following expression using Karnaugh – map  
 $f(A,B,C,D) = \sum m(1,4,7,10,13) + \sum d(5,14,15)$

- b) Give the gate-level realization for 8:1 mux with active-low enable input. Show how several 8:1 muxes can be combined to make a 32-to-1 mux. [5+5]

**OR**

- 5.a) Using the tabular method, obtain the prime implicants of a four- input single-output function  $f(w,x,y,z) = \sum m(0,2,4,5,6,7,8,9,10,11,13)$ . Reduce the prime-implicant table and find the minimal cover of f.

- b) Give the schematic circuit of a 2-to-4 binary decoder with an active-low enable input. Give the truth-table for the same. [5+5]



6.a) Draw the circuit diagram of a negative edge trigger J-K Flip-Flop with active high present and clear and explain its operation with the help of truth table.

b) Draw the circuit diagram of a mod-10 ripple counter and explain its operation with the aid of output state timing diagram. [5+5]

7.a) Draw the circuit diagram of a RS flip flop and explain its operation with the help of truth table.

b) Design a modulo 6 up/down synchronous counter using T flip-flops and draw the circuit diagram. [5+5]

8. A sequential circuit with 2 D flip-flops, A and B; 2 inputs, x and y; and one output z specified by the following equations.

$$A(t+1) = x'y + xA$$

$$B(t+1) = xB + xA$$

$$Z = B$$

a) Draw the logic diagram of the circuit

b) Derive the state table

c) Derive the state diagram. [3+3+4]

9. A combinational lock circuit has two imports ( $x_1, x_2$ ) and single output (Z) is to be designed such that the lock opens ( $z=1$ ) whenever there is a sequence of form consecutive input changes with  $x_2 = 1$ . Construct the state diagram and stable table for this circuit. [10]

10.a) What is meant by Tri-state logic? Draw the circuit of Tri-state TTL logic and explain its functions.

b) Discuss current sinking, current sourcing and noise margins of a standard TTL logic gate. [5+5]

OR

11.a) Draw the circuit diagram of basic TTL NAND gate and explain the three parts with the help of functional operation?

b) Describe CMOS driving TTL. [6+4]

---ooOoo---