

**Time: 3 Hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

**PART-A****(25 Marks)**

- 1.a) What is the main application of CC amplifier and Why? [2]
- b) What are the conditions for approximate h-parameter model? [3]
- c) What is base-spreading resistance? [2]
- d) What is the bypass capacitor and why it is connected in CE amplifier? [3]
- e) What is the effect of negative feedback on stability? [2]
- f) What is Barkhausen criterion? [3]
- g) What are the advantages of class-B operation? [2]
- h) What is harmonic distortion? [3]
- i) What are the properties of Q of a tuned circuit? [2]
- j) What is the effect of cascading on double tuned amplifier? [3]

**PART-B****(50 Marks)**

- 2.a) Draw the CC amplifier and derive the expression for  $A_i$ ,  $R_i$ ,  $A_v$ ,  $Y_o$ .
- b) A CE amplifier is drawn by a voltage source of internal resistance  $R_s = 800$  ohms and load impedance is a resistance  $R_L = 1000$  ohms. The h-parameters are  $h_{ie} = 1.0$  K ohms,  $h_{re} = 2 \times 10^{-4}$ ,  $h_{fe} = 50$  and  $h_{oe} = 25 \mu A/V$ . compute  $A_i$ ,  $R_i$ ,  $A_v$ ,  $R_o$  using exact analysis. [5+5]

**OR**

- 3.a) Derive the expression for the bandwidth of multistage amplifier.
- b) What is the use of transformer coupling in the output of multistage amplifier? [5+5]
- 4.a) Derive the equation for the lower 3dB frequency of CE configuration due to emitter bypass capacitor.
- b) Given the following transistor measurements made at  $I_C = 5$ mA and  $V_{CE} = 5$  V and at room temperature.  $h_{ie} = 600$  ohms,  $h_{re} = 100$ ,  $C_{b'e} = 3$ PF and  $A_i = 10$  at 10 MHz. Find  $f_\beta$ ,  $f_T$ ,  $C_{b'e}$ ,  $r_{b'e}$  and  $r_{bb'}$  of hybrid equivalent circuit in CE configuration. [5+5]

**OR**

- 5.a) Derive the expression for voltage gain of a common source FET amplifier with and without source resistance included in the circuit.
- b) In the CS amplifier  $R_L = 5$ K,  $R_G = 10$  Mohms,  $\mu = 50$  and  $r_d = 35$  K. Evaluate voltage gain, input impedance and output impedance. [5+5]

- 6.a) Show that bandwidth increases in negative feedback amplifiers.  
b) An amplifier has a input resistance of 200 K ohms, with a certain negative feedback introduced in the above amplifier the input resistance is found to be 20 M ohms and overall gain is found to be 1000. Calculate the loop gain and feedback factor. [5+5]

OR

- 7) Draw the circuit diagram of RC-Phase shift oscillator using BJT and derive the expressions for frequency of oscillations and condition on gain. [10]

- 8.a) Derive the expression for maximum conversion efficiency for a Transformer-coupled Class A power amplifier.

- b) List out the advantages of complementary symmetry configuration over push pull configuration. [7+3]

OR

- 9.a) Show that the maximum conversion efficiency of the idealized class B push-pull circuit is 78.5%.

- b) For an ideal class B transistor amplifier the collector supply voltage  $V_{cc}$  and the effective load resistance  $R_L = (N_1/N_2)^2 R_L$  are fixed as the base current excitation is varied. Show that the collector dissipation  $P_c$  is zero at no signal, rises as  $V_m$  increases and passes through a maximum at  $V_m = 2V_{cc}/\pi$ . [5+5]

- 10.a) Derive an expression for the bandwidth of a synchronous tuned circuit.

- b) Discuss the necessity of stabilization circuits in tuned amplifiers. [7+3]

OR

- 11) Draw the equivalent circuit of double tuned amplifier and derive the expression for gain at resonance. [10]

---ooOoo---