

Code No: 136FE

R16

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech III Year II Semester Examinations, May - 2019

INDUSTRIAL ELECTRONICS

(Common to EEE, ECE)

Time: 3 hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A. Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART - A

(25 Marks)

- 1.a) Write the need of differential amplifiers. [2]
- b) Write the ideal specifications of operational amplifiers. [3]
- c) Write the applications of servo voltage stabilizer. [2]
- d) Explain the role of current boosting in voltage regulators. [3]
- e) Write the applications of class A power amplifiers. [2]
- f) Draw and label characteristics of SCR. [3]
- g) Write the protection of SCR. [2]
- h) Explain about the static circuit breaker. [3]
- i) Name the different type of timers. [2]
- j) What is meant by the term welding? [3]

PART - B

(50 Marks)

- 2.a) Explain in detail about Darlington Emitter Follower.
- b) What are the advantages of differential amplifiers over normal common Emitter amplifier? [5+5]

OR

3. Explain the DC amplifier using emitter follower as the 1st stage and derive the expression for its gain using its equivalent circuit. [10]

4. How is short-circuit current protection provided for an IC regulator? Draw and explain the circuit diagram. [10]

OR

- 5.a) Explain about a voltage regulator circuit using LM 105 IC with an external pass transistor.
- b) What are the advantages of a current limiting circuit? [5+5]

6. Discuss briefly the different components of power loss that occur in a thyristor during its working. Which of the power loss components are dominant at power frequencies and which are dominant at high frequencies? [10]

OR

- 7.a) Draw and explain the waveforms of trigger pulse voltage and output voltage.
- b) Explain how SCR is used in triggering of thyristors. [5+5]

AG AG AG AG AG AG AG A

- 8.a) Explain different triggering modes of Triac and give comparison among them.
b) Discuss in detail about Firing Circuits.

[5+5]

OR

9. Discuss about the following:
a) Single transistor chopper
b) Two transistor chopper.

[5+5]

- 10.a) Explain the theory and principle of dielectric heating.
b) List various Industrial applications of dielectric heating.

[5+5]

OR

- 11.a) Write the merits and applications of High frequency heating.
b) Define the terms plastic welding and fusion welding.

[5+5]

---ooOoo---

AG AG AG AG AG AG AG A

AG AG AG AG AG AG AG A

AG AG AG AG AG AG AG A

AG AG AG AG AG AG AG A

AG AG AG AG AG AG AG A