

Code No: 154BH

R18

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech II Year II Semester Examinations, November/December - 2020

LINEAR IC APPLICATIONS

(Common to ECE, EIE)

Time: 2 Hours

Max. Marks: 75

Answer any Five Questions
All Questions Carry Equal Marks

- 1.a) Perform AC analysis of single input dual-output differential amplifier Configuration.
- b) List out the features of ideal OP-Amp. [10+5]
- 2.a) What are the differences between the inverting and non inverting terminals? What do you mean by the term "virtual ground"?
- b) List out AC and DC characteristics of OP-AMP. [7+8]
- 3.a) Draw the circuit diagram of instrumentation amplifier using 741 op-amp and explain its operation.
- b) How OP-AMP is used as integrator? Explain its working. [9+6]
- 4.a) How OP-AMP is used as Comparator? Explain its working.
- b) How OP-AMP is used as Arithmetic circuits? Explain its working. [6+9]
- 5.a) Design a active high pass filter with cutoff frequency of 4 KHz.
- b) Explain the working principle of Wein Oscillator. [7+8]
- 6.a) How to generate a Saw tooth waveform? Explain the working of such a circuit with a neat circuit diagram.
- b) Discuss in detail about band pass and band reject filters. [8+7]
- 7.a) Describe the 555 timer monostable multivibrator applications in:
i) Frequency divider ii) Pulse width modulation.
- b) Explain the terms frequency multiplication, frequency translation of PLL. [8+7]
- 8.a) What is the conversion time of a 10 bit successive approximation ADC if its input clock is 5 MHz?
- b) List and explain the specifications of DAC. [6+9]

---ooOoo---