

Code No: 133BJ

R16**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD****B.Tech II Year I Semester Examinations, April/May - 2018****NETWORK ANALYSIS****(Electronics and Communication Engineering)****Time: 3 Hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.


Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART- A**(25 Marks)**


- 1.a) Define Coefficient of Coupling and find the coefficient of coupling for two coils having $L_1=2$ H, $L_2=8$ H and $M= 3$ H? [2]
 b) Draw the impedance triangle and explain each term. [3]
 c) Define quality factor and band width of a series resonant circuit. [2]
 d) For the circuit shown in figure 1, if $v = 10e^{-4t}$ V and $i = 0.2e^{-4t}$ A, $t \geq 0$, find R and C. [3]

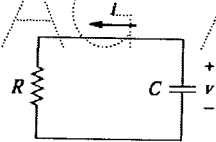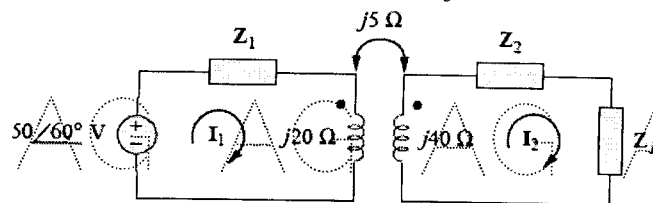**Figure 1**

- e) Define the following terms related to periodic function (i) RMS Value (ii) Average Value. [2]
 f) List any three properties of Laplace transform. [3]
 g) Write down the set of equations of a two port network in terms of ABCD parameters. [2]
 h) Define image and iterative impedance. [3]
 i) List the properties of Low Pass filter. [2]
 j) Explain about composite filters. [3]

PART-B**(50 Marks)**

- 2.a) In the circuit shown in figure 2, calculate the input impedance and current I_1 . Take $Z_1 = 60 + j100 \Omega$, $Z_2 = 30 + j40 \Omega$, and $Z_L = 80 + j60 \Omega$.

**Figure 2**

- b) For the network shown in figure 3 draw the oriented graph and frame the cut-set matrix. [5+5]

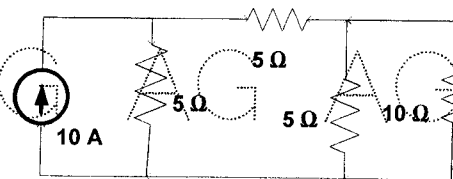


Figure 3
OR

- 3.a) Define Graph, Tree, Basic tie set matrix and cut set matrix for a planar network with an example.
b) Draw the oriented graph of a network with fundamental cut-set matrix as shown in figure 4. Also find number of cut-sets and draw them. [5+5]

Twigs				Links		
1	2	3	4	5	6	7
1	0	0	0	-1	0	0
0	1	0	0	1	0	1
0	0	1	0	0	1	1
0	0	0	1	0	1	0

Figure 4

- 4.a) Refer to the circuit shown figure 5 the switch is closed at $t = 0$. (i) determine equations for i_L and v_L . (ii) At $t = 300$ ms, open the switch and determine equations for i_L and v_L during the decay phase. (iii) Determine voltage and current at $t = 100$ ms and at $t = 350$ ms. (iv) Sketch i_L and v_L .

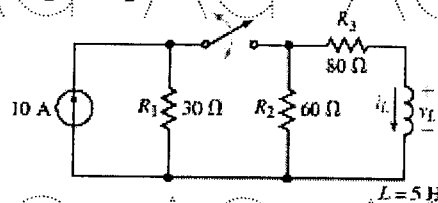


Figure 5

- b) A series resonant circuit has a bandwidth of 100 Hz and contains a 20 mH inductance and a 2 μ F capacitance. Determine (i) f_o (ii) Q (iii) Z_{in} at resonance (iv) f_2 . [5+5]

OR

- 5.a) Design a series RLC circuit that will have an impedance of 10Ω at the resonant frequency of $\omega_0 = 100 \text{ rad/s}$ and a quality factor of 80. Find the bandwidth.
- b) Consider the circuit shown in figure 6. Find $i(t)$ for $t < 0$ and $t > 0$. [5+5]

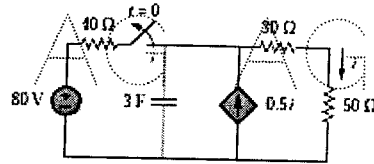


Figure 6

- 6.a) Obtain the response of R-L-C series circuit for exponential excitation. Use Laplace Transform method.
- b) Determine the RMS value of the current waveform shown in figure 7. If this current waveform is passed through 2Ω resistor find the average power absorbed by the resistor? [5+5]

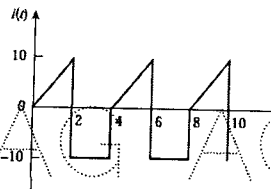


Figure 7

OR

- 7.a) A Voltage $V_m \sin(\omega t + \phi)$ is applied to an initially relaxed RL series circuit. Find the value of ϕ for which there will be no transient current in the circuit. Use Laplace Transform method.
- b) Find the-rms value of the voltage waveform shown in figure 8. [5+5]

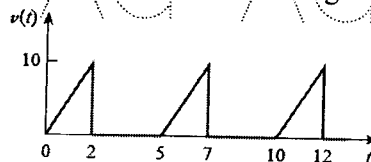


Figure 8

- 8.a) Obtain the y parameters for the circuit shown in figure 9.

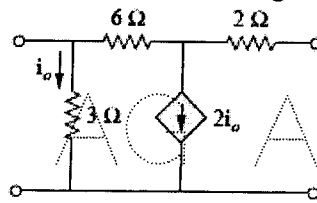


Figure 9

- b) For the network shown in figure 10 find the driving point input impedance and also plot the pole-zero patterns. [5+5]

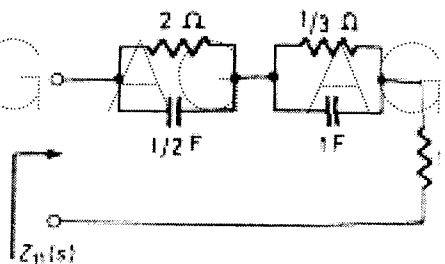


Figure 10
OR

- 9.a) Find the transfer function $G_{12}(s) = \frac{V_2(s)}{V_1(s)}$ for the network shown in figure 11.

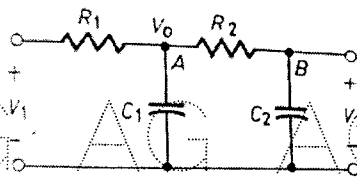


Figure 11

- b) Express hybrid parameters in terms of impedance parameters. [5+5]

- 10.a) An attenuator is composed of symmetrical T-section having series arm each of 175Ω and shunt arm of 350Ω . Derive expression for and calculate the characteristic impedance of this network and attenuation per section.

- b) Draw the circuit diagram of a Band pass filter? Explain the design procedure of the above filter in detail. [5+5]

OR

- 11.a) Design an asymmetrical T-attenuator to produce attenuation of 20 DB and to work between source impedance of 400Ω and load impedance of 900Ω .

- b) Classify the filters according to their
i) frequency characteristics and
ii) Depending upon the relation between series impedance and Shunt impedance. [5+5]

---oo0oo---