

**R18**

Code No: 153BH

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech II Year I Semester Examinations, December - 2019

NETWORK ANALYSIS AND TRANSMISSION LINES

(Electronics and Communication Engineering)

Time: 3 Hours

Max. Marks: 75


**Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A. Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b as sub questions.

**Note:** Provide a Smith chart.**PART - A**

(25 Marks)

- 1.a) What is graph of a network? Mention different types of graphs. [2]
- b) What is time constant? Explain with respect to series RL circuit. [2]
- c) Express ABCD for series network shown in figure 1. [2]

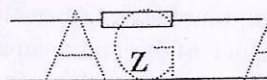
**Figure: 1**

- d) Evaluate the condition on inductor so as to achieve minimum attenuation on a transmission line. [2]
- e) How do you realize lumped elements using short circuit transmission lines? [2]
- f) Differentiate between planar and non planar graph. [3]
- g) A series resonant circuit has a bandwidth of 100 Hz and contains a 20mH inductance and a 2  $\mu$ F capacitance. Determine  $f_0$ , Q. [3]
- h) Design a  $\pi$  type attenuator with attenuation = 20dB and characteristic resistance = 600 $\Omega$ . [3]
- i) What is Group velocity? How is it different from phase velocity? [3]
- j) Enumerate the differences when smith chart is used as Z chart and Y chart. [3]

**PART - B**

(50 Marks)

- 2.a) Define incidence matrix. For the graph shown in figure 2, find the complete incidence matrix.

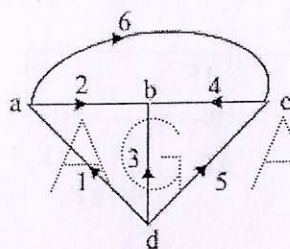**Figure: 2**

- b) Derive the equation for Equivalent inductance when two inductors are coupled in series opposing and mutual inductance exists between them. [6+4]

**OR**



- 3.a) Obtain an expression for coefficient of coupling.  
 b) Discuss dot convention used in magnetically coupled circuits. [5+5]

- 4.a) In a parallel Resonant circuit shown in figure 3, find the Resonant frequency, Dynamic impedance, Bandwidth, Q-factor and Current at resonance?

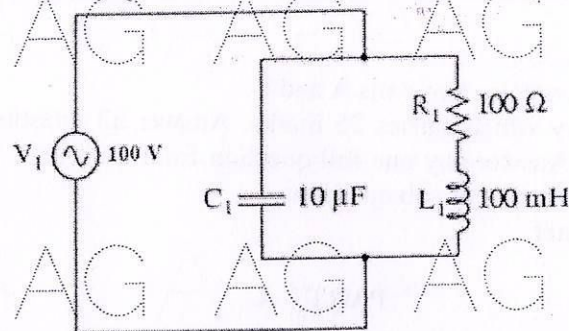


Figure: 3

- b) A coil has an inductance of 1.3 mH and resonates at 600 KHz and its  $Q = 30$ . If the bandwidth required is 50 kHz what resistor should be connected across the coil? [5+5]

OR

- 5.a) Derive the expression for bandwidth of series resonating circuit and its relation with  $Q$ .  
 b) An inductance of 0.5H, a resistance of  $5\Omega$  and a capacitance of  $8\mu\text{F}$  are in series across a 220V ac supply. Calculate the frequency at which the current flowing through the circuit becomes maximum. Also, find bandwidth, half power frequencies and voltage across capacitance at resonance. [5+5]

- 6.a) Express Y parameters in terms of hybrid parameters.  
 b) Find Y and Z parameters for the network of figure 4 which contains both dependent current and voltage source. [4+6]

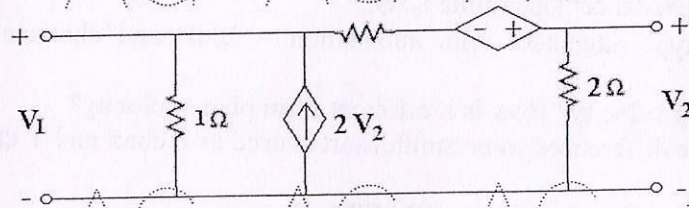


Figure: 4

OR

- 7.a) Apply the T- $\pi$  transformation to obtain an equivalent T network for the capacitive network given in the figure 5.

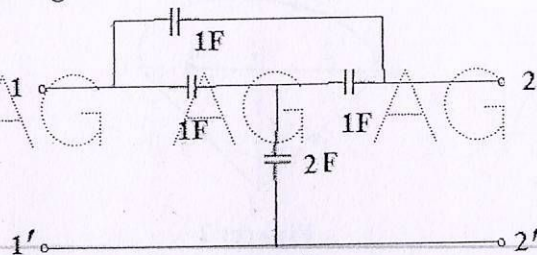


Figure: 5



- b) Find the ABCD parameters for the following circuit shown in figure 6.

[4+6]

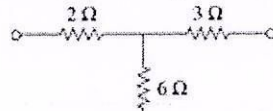


Figure: 6

- 8.a) Derive the transmission line equations in terms of sending and receiving end voltages and currents.
- b) The characteristic impedance of a 805 m long transmission line is  $94 \angle -23.2^\circ \Omega$ , the attenuation constant is  $74.5 \times 10^{-6} \text{ Np/m}$  and the phase shift constant is  $174 \times 10^{-6} \text{ rad/m}$  at 5 kHz. Calculate the line parameters R, L, G and C per meter and the phase velocity of the line.

[5+5]

OR

- 9.a) Explain in detail the distortions present on the transmission line. Derive the condition for distortionless line.
- b) The characteristic impedance of a low loss transmission line is  $90 \Omega$  and it is terminated by another impedance of  $(130 - j980) \Omega$ . The wavelength of the line is 2.6m. Determine the (i) VSWR (ii) Minimum and maximum impedance.
- 10.a) Write properties of  $\lambda/4$ ,  $\lambda/2$ ,  $\lambda/8$  line and mention applications of each line.
- b) A slotted line measurement yields the following parameter values. (i) Voltage minima at 9.2cm and 12.4cm measured away from the load with the line terminated in a short. (ii) VSWR=5.1 with line terminated in the unknown load, a voltage minima is located 11.6cm measured away from the load. Using smith chart calculate normalized load impedance.
- 11.a) What is single stub matching. Mention its types. Derive the expressions for length and location of stub to achieve impedance matching.
- b) The  $0.1\lambda$  length line has characteristic impedance of  $50 \Omega$  and is terminated with a load impedance of  $Z_L = 5 + j25 \Omega$  (i) locate  $Z_L = 0.1 + j0.5$  on the smith chart. (ii) What is impedance at  $l = 0.1\lambda$ . (use smith chart)

[5+5]

[4+6]

OR

[6+4]

---ooOop---