

Time: 3 Hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART- A


(25 Marks)

- 1.a) Draw transformed network (s-domain equivalent) for the series circuit having $R = 5 \Omega$, $L = 0.5 \text{ H}$ and $C = 0.5 \text{ F}$. [2]
- b) What do you understand by "Time Constant" of a circuit? What is its significance on the response of the circuit? [3]
- c) State the condition for symmetry and Reciprocity in a two port network in terms of 'h' parameters. [2]
- d) Obtain 'Z' parameters in terms of 'Y' parameters for a two port network. [3]
- e) Distinguish between a low pass filter and high pass filter. [2]
- f) Explain clearly about the Attenuation. [3]
- g) What are the uses of equalizer bar in DC generators? [2]
- h) What are the methods of speed control in DC motor? [3]
- i) Why is transformer rated in KVA? Justify. [2]
- j) How are the transformer losses affected if power factor of a given load is varied? [3]

PART-B

(50 Marks)

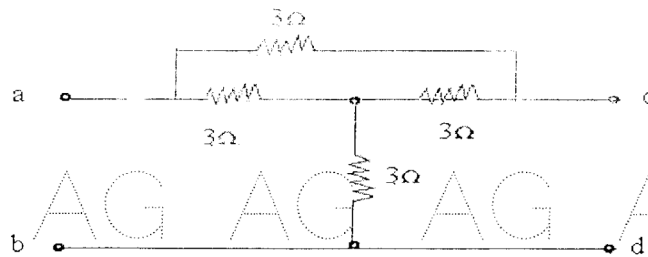2. A series RLC circuit with $R = 3 \Omega$, $L = 1 \text{ H}$ and $C = 0.5 \text{ F}$, is excited by a unit step voltage. Obtain the expression for $I(t)$ using Laplace Transform method. Assume that the circuit is initially relaxed. Sketch the variation of $I(t)$ and state whether the circuit is over damped, or under damped or critically damped. [10]
- OR**
- 3.a) Calculate the time taken by a capacitor of $1 \mu\text{F}$ and in series with a $1 \text{ M}\Omega$ resistance to be charged up to 80% of the final value.
- b) In a series RL circuit, the application of a dc voltage results in a current of 0.741 times the final steady state value of current after 1 sec. However, after the current has reached its final value, the source is short circuited. What would be the value of current after one second? [5+5]
4. Define ABCD parameters of a two port network and obtain the relation with Z-parameters. Determine Y-parameters for the bridge- T network shown in figure. [10]



OR

- 5.a) What is a transformed network? Explain clearly with an example.
 b) The Voltages at the two ports of a two-port network are represented as $V_1 = 5I_1 + 5I_2$, $V_2 = I_1 + 2I_2$. If a load impedance of $3\angle 0^\circ$ ohm is connected at the output port, determine the input impedance. [5+5]
6. Design a constant K, T-section and π -section high pass filter having cut off frequency $f_c = 10$ kHz and characteristic impedance $Z_0 = 500$ ohms. Calculate: a) the characteristic impedance and phase constant of the filter at 25 kHz and b) attenuation of the filter at 5 kHz. [10]

OR

- 7.a) Bring out the drawbacks of constant K filters.
 b) Obtain the necessary equations for a m-derived T-section low pass filter from a proto type constant K-filter. [4+6]

- 8.a) Derive the induced e.m.f equation of a D.C. Generator.
 b) The armature of a 4-pole, lap-wound DC shunt generator has 120 slots with 4 conductors per slot. The flux per pole is 0.05wb. The armature resistance is 0.05-ohm and the shunt field resistance is 50 ohms. Then find the speed of the machine when supplying 45A at terminal voltage of 250V. [5+5]

OR

- 9.a) Explain the magnetizing characteristics of DC shunt generator.
 b) A 4 pole lap wound D. C. shunt generator has a useful flux per pole of 0.07 wb. The armature winding consists of 220-turns each of 0.004 ohms resistance. Calculate the terminal voltage when running at 900 rpm if the armature current is 50A. [5+5]

- 10.a) Obtain the equivalent circuit of a single phase transformer referred to LV side and HV side.

- b) A single phase 50Hz transformer has 100 turns on the primary and 400 turns on the secondary winding. The net cross sectional area of core is 250 cm^2 . If the primary winding is connected to a 230V 50Hz supply, determine
 i) The EMF induced in the secondary winding
 ii) The maximum value of flux density in the core. [5+5]

OR

- 11.a) Explain the principle of operation of a transformer. Derive its emf equation.
 b) A single phase transformer has 180 and 40 turns respectively in its secondary and primary windings. The respective resistances are 0.233 and 0.067 Ω . Calculate the equivalent resistance of i) the primary in terms of the secondary winding ii) the secondary in terms of the primary winding. [5+5]

---ooOoo---