

Code No: 153AC

R18

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year I Semester Examinations, March - 2021

ANALOG ELECTRONICS
(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- 1.a) What is PN junction diode? Explain the working of PN junction under forward bias and reverse bias with neat diagram.
b) Explain the operation of a negative clipper with neat sketches. [10+5]
- 2.a) Draw the input and output characteristics of a NPN transistor in CB configuration and explain.
b) Compare Half Wave and Full Wave Rectifiers. [10+5]
- 3.a) Draw the high frequency equivalent circuit of CS amplifier and derive the expressions for voltage gain, input and output impedance.
b) Discuss MOSFET as a switch. [10+5]
- 4.a) Draw the circuit diagram of transformer coupled class-A power amplifier and explain its operation. Also derive the expression of conversion efficiency.
b) What are the limitations of single stage amplifiers and how are they overcome in multistage amplifiers? [10+5]
- 5.a) Draw the circuit diagram of Hartley oscillator, derive the expression for frequency of oscillation.
b) For the voltage series feedback amplifier, derive the expression for gain, input resistance. [8+7]
- 6.a) Explain different coupling schemes used in multistage amplifiers with their frequency response.
b) Calculate the gain, input impedance, output impedance of voltage series feedback amplifier having $A=-300$, $R_i=1.5K$, $R_o=50K$ and $\beta=-1/20$. [10+5]
- 7.a) Explain the following in detail:
i) Input offset voltage ii) Input offset current iii) CMRR iv) Slew Rate.
b) With the help of a circuit diagram explain the functioning of square wave generator. [8+7]
- 8.a) List the characteristics of an Ideal operational amplifier.
b) Derive the transconductance g_m and drain resistance r_d of Field Effect Transistor small signal model. [6+9]

---ooOoo---