

Code No: 153AC

R18

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year I Semester Examinations, October - 2020

ANALOG ELECTRONICS

(Electrical and Electronics Engineering)

Time: 2 hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- 1.a) Explain DC load line and Q point for any transistor configuration. Also state the necessity of biasing and list biasing methods for transistor. [8+7]
b) Explain positive and negative clippers.
- 2.a) Draw and explain output characteristics of CE configuration. [7+8]
b) Explain with neat figures the function of a half wave rectifier.
- 3.a) Explain the working of N-channel E-MOSFET.
b) Explain about MOSFET CG amplifier and derive the expression for gain, input impedance output impedance. [6+9]
- 4.a) Describe the small signal equivalent circuit of the MOSFET and determine the values of Small signal parameters. [9+6]
b) Compare in detail about CD and CG amplifier.
- 5.a) For a class B power amplifier using a supply voltage of $V_{cc} = 12V$, and driving a load of 80Ω , Determine the maximum load power, DC input power and collector efficiency. [9+6]
b) Discuss the need for cascading amplifiers.
- 6.a) Derive an equation for power output and conversion efficiency of a class A Direct coupled amplifier. [8+7]
b) Define Coupling. Describe different types of coupling multistage amplifiers in detail.
- 7.a) Explain current series feedback amplifier.
b) The RC network of a Wein bridge oscillator consists of resistors and capacitors of values $R_1=R_2=220\text{ k}\Omega$ and $C_1=C_2=250\text{ PF}$. Determine the frequency of oscillations. [10+5]
- 8.a) Discuss the functioning of a practical integrator and derive the necessary expression.
b) Derive the expression for voltage gain of a non-inverting amplifier. [8+7]