

Code No: 124A

133

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year II Semester Examinations, May - 2017

ELECTRONIC CIRCUITS

(Electrical and Electronics Engineering)

Time: 3 Hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART-A

(25 Marks)

- 1.a) Which configuration in BJT provides the Current gain? [2]
- b) How amplifiers are classified according to the type of transistor configuration? [3]
- c) What the term f_p indicates at high frequency? [2]
- d) What is Frequency Distortion? [3]
- e) Distinguish between comparators and clipping circuits. [2]
- f) What are the applications of Schmitt trigger? [3]
- g) Explain the operation of Heat sinks. [2]
- h) Why RC circuits are commonly used compared to RL circuits? [3]
- i) How does diode acts as a switch? [2]
- j) Name the technologies which use bipolar transistors. [3]

PART-B

(50 Marks)

2. Draw the circuit of an emitter follower, and derive the expressions for A_v , A_v , R_i , R_o in terms of CE parameters. [10]

OR

3. Determine the effect of negative feedback on the input and output impedances of a Voltage-Series feedback amplifier. Show the circuit schematic diagram. [10]

- 4.a) Draw the ideal and actual frequency response curves of single stage amplifiers.

- b) Write a short note on Design of High frequency Amplifiers. [5+5]

OR

- 5.a) Draw and explain the FET high frequency model.

- b) Write a short note on Low frequency response of BJT amplifiers. [5+5]

- 6.a) With help of neat circuit diagram and waveforms, explain the working of a collector coupled Monostable multivibrator.

- b) Why commutating capacitors are used in Multivibrators? [7+3]

OR

- 7.a) Draw a circuit using diodes to transmit that part of a sine wave which lies between -4V and -7V.

- b) With the help of a neat diagram, explain the working of an emitter-coupled clipper. [5+5]

- 8.a) Draw the ideal and actual frequency response curves of single stage amplifiers.

- b) Write a short note on Design of High frequency Amplifiers.

OR

- 9.a) Draw and explain the FET high frequency model.

- b) Write a short note on Low frequency response of BJT amplifiers.

10. a) With help of neat circuit diagram and waveforms, explain the working of a collector coupled Monostable multivibrator.

- b) Why commutating capacitors are used in Multivibrators? [7+3]

AG AG AG AG AG AG AG A

8.a) Explain the high pass RC circuit response for sinusoidal input and derive expression for cut-off frequency.

b) Discuss the concept of Thermal Runway. [6+4]

9. **OR**
Draw the circuit diagram of Class-B Complementary Push-Pull Amplifier and explain its working and derive the expression for maximum conversion efficiency. [10]

10.a) Explain the operation of transistor switch in saturation.

b) Write a short note on piecewise linear diode characteristics. [5+5]

OR

11.a) Explain the Break down voltage consideration of transistor.
b) Discuss about saturation parameters of Transistor and their variation with temperature. [5+5]

---ooOoo---

8.10 Explain the high pass RC circuit response for sinusoidal input and derive expression for

AG AG AG AG AG AG AG A

AG AG AG AG AG AG AG A

AG AG AG AG AG AG AG A

AG AG AG AG AG AG AG A

AG AG AG AG AG AG AG A