

Code No: 115AH

R13

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech III Year I Semester Examinations, November/December - 2016

IC APPLICATIONS

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A. Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART - A

(25 Marks)

- 1.a) Explain "Latch up" and the circumstances it needed. [2]
- b) Discuss how a logic buffer amplifier is different from an audio amplifier. [3]
- c) List the features of 741 OP-AMP. [2]
- d) List the non-ideal DC characteristics of an OP-AMP. [3]
- e) What is frequency stability? Explain its significance. [2]
- f) What is an Active filter? What are the advantages offered by it over a passive filter? [3]
- g) What are the modes of operation of a Timer? [2]
- h) What is the major difference between digital and analog PLLs? And list the applications of PLL. [3]
- i) How many resistors are required in a 12-bit weighted resistor DAC? Why? [2]
- j) Explain how Dual-slope ADC provides noise rejection? [3]

PART - B

(50 Marks)

- 2.a) Compare the TTL and CMOS logic families.
  - b) Design a TTL 2-state NAND gate and explain its operation. [4+6]
- OR
- 3.a) What is interfacing? Explain the operation of TTL driving CMOS.
  - b) Explain the operation of the TTL open collector outputs. [5+5]
- 4.a) What is instrumentation amplifier? What are the features of it? Explain any three applications of instrumentation amplifier.
  - b) Derive input resistance for inverting amplifier with feedback arrangement. [4+6]
- OR
- 5.a) Discuss how a voltage follower is built using an op-amp.
  - b) In an AC inverting amplifier circuit  $R_{in}=50\Omega$ ,  $C_i=0.1\mu F$ ,  $R_1=100K\Omega$ ,  $R_f=1K\Omega$ ,  $R_2=10K\Omega$  and  $V_{cc}=\pm 15V$ . Determine the Bandwidth of the amplifier. [4+6]

- 6.a) Derive the expression for the transfer function of first order high pass filter.  
 b) Draw the schematic diagram of Wein bridge oscillator and explain its working. [6+4]

OR

- 7.a) Design a first order active high pass filter with cutoff frequency of 2KHz with op-amp. Why this is called Active filter?  
 b) Design a Triangular wave generator with  $f_0 = 1.5$  KHz and  $V_0 (PP) = 5V$ . [5+5]

- 8.a) Describe the 555 timer monostable multivibrator applications in pulse stretching.  
 b) Design a 555 timer circuit whose output frequency is 2KHz when the trigger input signal frequency is 4KHz. [5+5]

OR

- 9.a) Explain the operation of frequency multiplier using PLL.  
 b) Define Lock-in range, Capture range and Pull-in time in PLL system. [6+4]

- 10.a) Compare the dual slope ADC with successive approximation ADC.  
 b) Explain the operation of R-2R ladder DAC with the help of neat diagrams. [4+6]

OR

- 11.a) Explain the operation of flash ADC using relevant diagrams.  
 b) What are the merits and demerits of counter type ADC? Explain. [6+4]

---ooOoo---

P6 P6 P6 P6 P6 P6 P6  
 P6 P6 P6 P6 P6 P6 P6  
 P6 P6 P6 P6 P6 P6 P6  
 P6 P6 P6 P6 P6 P6 P6  
 P6 P6 P6 P6 P6 P6 P6