

Code No: 115AH

R13

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech III Year I Semester Examinations, February/March - 2016

IC APPLICATIONS

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 75

Note: This question paper contains two parts A and B.
Part A is compulsory which carries 25 marks. Answer all questions in Part A.
Part B consists of 5 Units. Answer any one full question from each unit.
Each question carries 10 marks and may have a, b, c as sub questions.

Part- A

(25 Marks)

- 1.a) Draw the interfacing circuit of CMOS driving TTL gate. [2]
- b) Why Integrated circuits are needed? [3]
- c) List all ideal characteristics of Op-amp. [2]
- d) What is the effect of negative feedback in non-inverting amplifier? [3]
- e) What are the advantages of active filters? [2]
- f) What is VCO? Discuss. [3]
- g) What are the basic building blocks of PLI? [2]
- h) What are the basic differences between the two operating modes of the 555 timer? [3]
- i) What is the advantage of R-2R ladder D-A converter over the one with binary weighted resistors? [2]
- j) What are the different types of ADCs and compare them in terms of speed of operation. [3]

Part-B

(50 Marks)

2. Draw the circuit diagram of TTL NAND gate and explain its working with the help of functional table. [10]

OR

3. Draw the circuit diagram of CMOS transmission gate and explain its working. [10]
- 4.a) The op-amp is configured as an inverting amplifier with $R_i = 1\text{k}\Omega$ and $R_f = 10\text{k}\Omega$. Calculate exact closed loop gain, ideal closed loop gain and compare these two results.
- b) Draw the differential amplifier circuit using op-amp and explain its working. [5+5]

OR

- 5.a) Design a subtractor circuit whose output is equal to the difference between the two inputs. Use a basic differential op-amp configuration.
- b) Draw the circuit diagram of an Instrumentation amplifier and explain its working. [5+5]
6. Design a second order High pass active filter with cutoff frequency of 2 kHz and also draw its frequency response. [10]

OR

7. Draw the circuit diagram of quadrature oscillator and derive the equation for frequency of oscillations and also design such a circuit to generate oscillations at a frequency of 159 Hz. [10]
- 8.a) Draw the functional block diagram of 555 timer and explain its operation.
- b) What are the applications of 555 timer and explain any one application in detail. [5+5]

OR

- 9.a) Explain the role of Low pass filter and VCO in PLL.
b) How PLL is used for frequency multiplier? Explain. [5+5]
- 10.a) For the D.A converter using an R-2R ladder network, determine the size of each step if $R_f = 27k\Omega$ and $R = 10k\Omega$ and also calculate the output voltage when the inputs b_0, b_1, b_2 and b_3 are at 5V.
b) Draw the circuit diagram of binary-weighted resistor DAC and explain its working. [5+5]

OR

- 11.a) Draw the circuit diagram of Dual slope ADC and explain its working.
b) What is the role of DAC in successive approximation ADC? [5+5]

--ooOoo--