

AG AG AG AG AG AG AG A

**R16**

Code No: 136CH

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech III Year II Semester Examinations, November/December - 2020

LINEAR AND DIGITAL IC APPLICATIONS

(Electrical and Electronics Engineering)

AG AG

AG AG A

Time: 2 hours

Max. Marks: 75

Answer any five questions  
All questions carry equal marks

---

1.a) Draw the circuit diagram of an instrumentation amplifier using op-amp with its operation. [10+5] A

b) What are the features of IC 741? [10+5]

2.a) With neat circuit diagram explain the working principle of IC 723 voltage regulator. [8+7]

b) What is slew rate? Discuss the methods of improving slew rate. [8+7]

3.a) Design and draw the square wave generator using op-amp and explain its operation. [8+7]

b) Design a first-order active low pass filter such that it has a cut off frequency of 2 kHz and pass Band gain of '1' [8+7] A

4.a) Draw the block schematic of PLL and explain the operation of each block. [8+7]

b) Design an Astable Multivibrator using 555 Timer to produce 1 KHz square wave for duty cycle=0.5. [8+7]

5.a) Discuss about the working of R-2R Ladder D-to-A Converter with neat circuit diagram. [10+5] A

b) What are the limitations of weighted resistor type D/A converter? [10+5]

6.a) Explain the operation of Successive approximation A-to-D Converter. [10+5]

b) Explain in brief stability of a converter. [10+5]

7.a) With suitable example, explain how CMOS logic driven by TTL logic. [8+7]

b) Design a 32:1 mux using 74x151 IC and draw its logic diagram. [8+7] A

8.a) Design a 4-bit bidirectional shift register with parallel load. [8+7]

b) Explain the working of 4 bit asynchronous counter using ICs. [8+7]

AG AG AG AG AG AG AG A

---ooOoo---

AG AG AG AG AG AG AG A