

AG AG AG AG AG AG AG A

R16

Code No: 136DJ

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech III Year II Semester Examinations, November/December - 2020

AG AG AG AG AG AG AG A

POWER ELECTRONICS
(Electrical and Electronics Engineering)

Time: 2 Hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

1. Explain the working of IGBT. [15]
2. Explain the dynamic characteristics of SCR with necessary waveforms. [15]
- 3.a) A single phase 230 V, 1 kW heater is connected across single phase 230 V 50 Hz supply through an SCR. For firing angle delay of 45 degrees and 90 degrees, calculate the power absorbed in the heater element.
- b) Explain the effect of source inductance in a single phase full converter. [7+8]
4. Explain the working of three phase semi-converter for a firing delay angle of 45 degree. [15]
5. The three-phase full-wave A. C. voltage controller supplies a Y-connected resistive load of $R = 10$ Ohms and the line-to-line input voltage is 208 V (rms), 60 Hz. The delay angle is $\pi/3$. Determine a) the rms output phase voltage V_o , b) the input PF, and (c) the expression for the instantaneous output voltage of phase a . [5+5+5]
6. A single-phase full-wave ac voltage controller has a resistive load of $R = 10$ Ohms and the input voltage is $V_s = 120$ V (rms), 60 Hz. The delay angles of thyristors T_1 and T_2 are equal to 90 degrees. Determine (a) the rms output voltage V_o , (b) the input PF, (c) the average current of thyristors I_A , and (d) the rms current of thyristors. [4+4+4+3]
7. Explain the working of AC chopper with necessary circuits and waveforms. [15]
8. Explain the working of series inverter and modified series inverter with necessary waveforms and circuits. [15]

---ooOoo---

AG AG AG AG AG AG AG A

AG AG AG AG AG AG AG A