

AG AG AG AG AG AG AG

R18

Code No: 156CJ

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech III Year II Semester Examinations, August/September - 2021

POWER SEMICONDUCTOR DRIVES

(Electrical and Electronics Engineering)

Time: 3 Hours

Max. Marks: 75

Answer any five questions

All questions carry equal marks

1. Analyze the motoring and plugging operating modes of a separately excited DC motor when it is supplied by single phase fully controlled converter. [15]
2. Explain the operation of a three-phase fully controlled rectifier fed DC series motor for continuous conduction, also draw the voltage and current waveforms when firing angle is 30° . [15]
3. Discuss about four Quadrant Operation of DC Drives by single phase dual converter. [15]
4. Explain the operation of four quadrant chopper feeding to a DC series motor and draw the wave forms for continuous current operation. [15]
- 5.a) Compare VSI and CSI operations.
b) Explain the closed loop operation of induction motor drive with block diagrams. [6+9]
6. Explain the operation and control of Induction motor by AC voltage controller. [15]
7. Sketch a suitable diagram and explain the working of slip-power recovery system using Static Scherbius drive. [15]
8. With a suitable diagram explain the closed loop operation of synchronous motor drive. [15]

—ooOoo—

AG AG AG AG AG AG AG

AG AG AG AG AG AG AG