



Question Paper Code:

EE103ES

ACE-R20

**Supplementary Examination**  
**I B. Tech- I Semester- November 2021**  
**BASIC ELECTRICAL ENGINEERING**  
**(Common To EEE,CSE,IT,CSD)**

Time: 3 Hours

Max. Marks: 70

H. T. No

*Answer any five full questions from the following. All Questions carry equal marks.*  
M=Marks; CO=Course Outcomes; PO= Program Outcomes

Q.No	Question	M	CO	PO
1. a)	State and Explain Superposition Theorem.	7	1	1,2
b)	Find current Through 6 Ω Resistor using Superposition Theorem?	7	1	1,4
2. a)	Explain with neat diagrams Ideal Voltage source and Practical Voltage source.	7	1	2
b)	State and Explain Thevenin's Theorem with appropriate circuit.	7	1	1,2
3. a)	Sketch the Sinusoidal alternating waveform and Define: (i) Instantaneous value (ii) Waveform (iii) Cycle (iv) Frequency. (v) Time Period (vi) Amplitude.	7	2	1,2
b)	Derive the expression for root mean square value of an alternating sinusoidal current wave form $I = I_m \sin \theta$	7	2	1,4
4. a)	(a) Sketch and Explain the phasor diagram of RLC series circuit for i) $X_c > X_L$ (ii) $X_c < X_L$ , (iii) $X_c = X_L$ .	7	2	1,4
b)	A reactor having negligible resistance and an inductance of 0.1 H is connected in series with a resistor of 15 Ohms. The circuit is connected across a 230 V, 50 Hz, Single phase AC supply. Find i) Current flowing through the circuit ii) Power factor of the circuit iii) Voltage across the reactor.	7	2	1,4
5. a)	Prove that the Efficiency of a Transformer is Maximum when Variable losses equal to constant losses.	7	3	1,2
b)	Explain the Principle of Transformer and losses that occur in a Transformer.	7	3	1,2
6. a)	Explain the Working principle of a D.C Generator with a neat sketch.	7	4	1,2

b)	A 6 pole, Lap Wound armature has 840 conductors and flux per pole of 0.018 Wb. Calculate the emf generated, When the machine is running at 600 rpm.	7	4	1,2
7. a)	Explain with the help of diagrams , How a rotating magnetic field is produced in a 3 phase Induction Motor?	7	4	1,2
b)	Explain the working of a Synchronous motor. Give the constructional features of a Synchronous motor.	7	4	
8. a)	Explain the following terms i) Switch fuse unit ii) MCB iii) MCCB iv) ELCB	7	5	1,3
b)	Compare Between Primary and Secondary Batteries.	7	5	1,3