

**R18**

Code No: 153AC

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**

**B. Tech II Year I Semester Examinations, March - 2022**

**ANALOG ELECTRONICS**  
(Electrical and Electronics Engineering)

Time: 3 Hours

Max. Marks: 75

**Answer any five questions**  
**All questions carry equal marks**

--

- 1.a) How does the reverse saturation current of a diode and voltage varies with temperature? Explain. [6+9]  
b) Derive the expressions for the following parameters of the half wave rectifier circuit:  
i) Average DC current ii) RMS value of current iii) Rectifier efficiency. [6+9]
- 2.a) Discuss the self bias circuit and derive the expression for S? [7+8]  
b) Explain the drain characteristics of depletion MOSFET. [7+8]
- 3.a) Explain the small signal model of CS MOSFET amplifier. Also derive the expression for amplification factor. [10+5]  
b) Write short note on MOSFET as a resistor. [10+5]
- 4.a) Explain the working of common emitter direct coupled amplifier. [7+8]  
b) Prove that class B push pull amplifier efficiency is 78.5%. [7+8]
- 5.a) Derive the voltage gain for unbalanced output differential amplifier. [7+8]  
b) Explain the operation direct coupled class-A power amplifier. [7+8]
- 6.a) Draw the circuit of current series feedback amplifier and derive the expressions for input and output resistances. [10+5]  
b) Why are RC oscillators preferred for the generation of low frequencies? [10+5]
- 7.a) Calculate the gain, input impedance and output impedance of voltage series feedback amplifier having  $A = -300$ ,  $R_i = 50K\Omega$  and  $\infty = -1/20$ . [7+8]  
b) Explain non inverting op-amp circuit. [7+8]
- 8.a) Construct an op-amp integrator circuit to and explain. [8+7]  
b) Explain differential amplifier using one op-amp. [8+7]

---ooOoo---