

Code No: 155CB

**R18**

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**

**B. Tech III Year I Semester Examinations, February - 2022**

**MEASUREMENTS AND INSTRUMENTATION**

**(Electrical and Electronics Engineering)**

**Time: 3 hours**

**Max. Marks: 75**

**Answer any five questions  
All questions carry equal marks**

---

- 1.a) A moving coil instrument gives a full-scale deflection of 10mA when the potential difference across its terminal is 100mV. Calculate,  
i) The shunt resistance for a full-scale deflection of 100A  
ii) Find the resistance for full-scale reading with 100V  
Also, calculate the power dissipation in each case.

b) Derive an equation for the torque developed in PMMC instrument. [8+7]

- 2.a) A PMMC ammeter has following specification, coil dimension of 1cm×1cm, spring constant is  $0.15 \times 10^{-6}$  N-m/rad, Flux density is  $1.5 \times 10^{-3}$  wb/m<sup>2</sup>. Determine the number of turns required to produce a deflection of 90°, when a current of 2mA flows through the coil.

b) With the help of a neat diagram, explain the working of attracted disc type voltmeter. [7+8]

- 3.a) Discuss how AC potentiometer can be used for calibration of wattmeter.

b) Explain the procedure to calibrate voltmeter and ammeter using DC potentiometer. [8+7]

- 4.a) With help of a neat diagram explain the working of coordinate type potentiometer.

b) Draw the equivalent circuit diagram and phasor diagram of the current transformer. [8+7]

- 5.a) Discuss the construction and Working Principle of Electrodynamicometer type 1-φ wattmeter with help of a neat diagram.

b) Explain any two errors that occur in electrodynamicometer type 1-φ wattmeter and its compensation. [9+6]

- 6.a) With help of a neat diagram, explain the construction and working of a three-phase energy meter.

b) Two-watt meters are connected to measure the input to a balanced 3 phase circuit indicating 2000W and 500W respectively. Find the power factor of a circuit.

- i) When both the reading is positive and  
ii) When the latter reading is obtained after reversing the connections to the current coil of the first instrument. [9+6]

AG AG AG AG AG AG AG A

7.a) Draw the circuit of Kelvin double bridge used for measurement of low resistance. Explain its working principle

b) An AC bridge is balanced at 2KHz with the following components in each arm: Arm AB=10K $\Omega$ , Arm BC=100 $\mu$ F in series with 100K $\Omega$ , Arm AD=50K $\Omega$ . Find the unknown impedance  $R \pm jX$  in the arm DC, if the detector is between BD. [8+7]

8.a) Derive an equation for gauge factor in strain gauge.

b) With help of a neat diagram, explain the principle and working of LVDT. [7+8]

AG AG AG AG AG AG AG A  
---ooOoo---

AG AG AG AG AG AG AG A

AG AG AG AG AG AG AG A

AG AG AG AG AG AG AG A

AG AG AG AG AG AG AG A

AG AG AG AG AG AG AG A