

Code No: 153BH

R18

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech II Year I Semester Examinations, March - 2022

NETWORK ANALYSIS AND TRANSMISSION LINES

(Electronics and Communication Engineering)

Time: 3 Hours

Max. Marks: 75

Answer any five questions

All questions carry equal marks

---

1. Explain the following terms:  
a) Graph of a network  
b) Oriented Graph  
c) Rank of a Graph  
d) Planar and non-planar graph and  
e) Subgraph. [15]
2. Calculate the currents  $I_1$  and  $I_2$  for the following circuit shown in figure 1. [15]

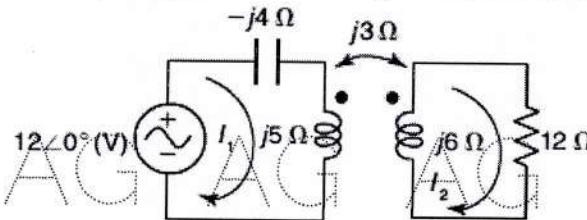


Figure: 1

- 3.a) Prove that the active power consumed in any purely reactive circuit is zero.
- b) For the following network shown in figure 2, a steady state is reached with switch open. At  $t = 0^-$ , switch is closed. Find the three loop currents at  $t = 0^+$ . [6+9]

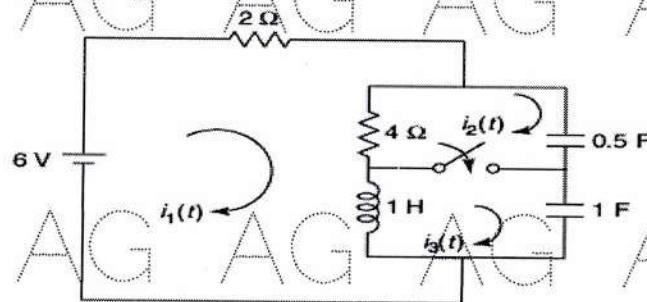


Figure: 2

4. For the circuit shown in figure 3, find  $i_1(t)$  for  $\omega = 100$  rad / sec. [15]

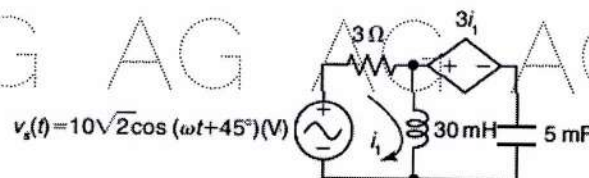


Figure: 3

- 5.a) Explain the condition for symmetry in a two port network with a proper example.  
 b) For the following network shown in figure 4, find the Y – parameters. [6+9]

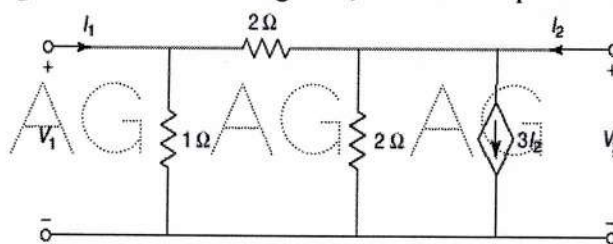


Figure: 4

6. What are image parameters? Derive expression of image parameters in terms of:  
 a) ABCD parameters  
 b) open-circuit and short-circuit impedances. [7+8]

7. The values of primary constants of an open-wire line per km are  $R = 10 \Omega$ ,  $L = 3.5 \text{ mH}$ ,  $C = 0.008 \mu\text{F}$  and  $G = 0.7 \mu\text{S}$ . For a signal frequency of 1000 Hz, calculate the characteristic impedance, Propagation constant, attenuation constant, phase constant, wavelength and phase velocity  $v_p$ . [15]

- 8.a) List and explain the characteristics of impedance smith chart.  
 b) Explain the significance and design of single stub impedance matching and discuss the factors on which stub length depends. [7+8]

---ooOoo---