

An AUTONOMOUS Institution

Question Paper Code:

EE103ES

ACE-R20

Semester End Examination I B. Tech- I Semester Regular/ Supply -JUNE-2022 Basic Electrical Engineering (Common to EEE, CSE, IT,CSD)

Time: 3 Hours

(

Max. Marks: 70

H. T. No	
----------	--

Answer any 5 Questions out of 8 Questions from the following Marks Question Q.No Obtain the expressions for star-delta and delta-star equivalence of resistive network 7 1. a) 7 What are active and passive elements? Explain in detail. b) 2. a) A coil takes a current of 1 A at 0.6 lagging power factor from a 220 V, 60 Hz single-phase source. If the coil is modeled by a series RL circuit, find, (i) The complex power in the coil and (ii) The values of R and L. What is series resonance? Derive the expression for resonant frequency? b) Explain in detail about construction and working principle of a Single-phase 14 3. transformer. 8 What are the losses present in the transformer and how these can be reduced? 4. a) 6 Find the equivalent resistance R_{ab} between terminals a and b Analyze the RL and RC circuits with AC input and find the current equations. Draw 6 5. a) the phasor diagrams 8 A series R L C Circuit with R=10Ω,L=10mH and C=100μF is excited by a single phase 230V, 50Hz supply. Determine the total current, voltages across R,L and C elements

6. a)	Explain how the speed of a Separately Excited DC motor can be controlled	7
b)	Explain the construction of the DC Generator with a neat sketch.	7
7. a)	What are the types of batteries and explain about important characteristics of	6
	batteries?	
b)	Explain about the following	8
	i) MCB ii)MCCB iii) Earthing iv) Types of batteries	
8. a)	Explain the construction and working principle of a single-phase induction motor.	7
b)	Explain the construction of synchronous generator.	7

