



ACE
Engineering College
(with a Difference in Excellence)

An AUTONOMOUS Institution



Question Paper Code:

EE302PC

ACE-R20

Semester End Examination
II B. Tech- I Semester- MARCH-2022
ELECTRICAL CIRCUITS
(Electrical and Electronics Engineering)



Time: 3 Hours

Max. Marks: 70

H. T. No										
----------	--	--	--	--	--	--	--	--	--	--

Answer any 5 Questions out of 8 Questions from the following

Q.No	Question	Marks
1. a)	<p>Determine the current flowing through the 6Ω resistor and voltage drop across 2Ω resistor in the circuit shown below figure by using nodal analysis.</p>	6
b)	<p>Find V_o in the circuit shown in below figure by using Thevenin's Theorem.</p>	8
2. a)	<p>Explain reciprocity theorem in detail.</p>	6
b)	<p>Compute the v_o using super position theorem for the circuit shown in figure.</p>	8
3.	<p>Derive the expression for the complete response for current in a series RLC circuit excited by DC supply by closing the switch at $t=0^+$</p>	14

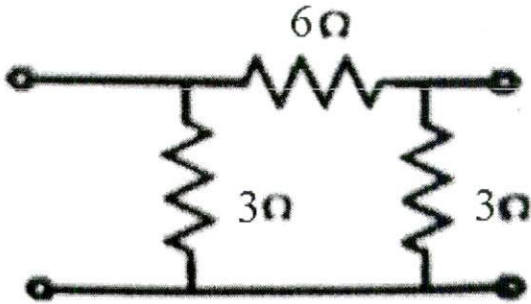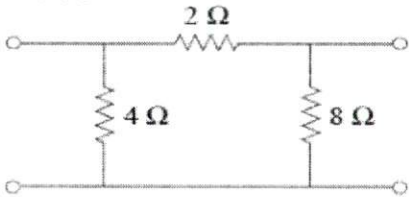4.	<p>Explain the following</p> <p>a) Dot convention in coupled circuits</p> <p>b) Ideal transformer</p> <p>c) Complex power in a 1-ϕ circuit</p>	5+5+4
5. a)	Evaluate the DC transient response of RL series circuit.	7
b)	Deduce the expression for co-efficient of coupling of a magnetically coupled circuit.	7
6. a)	Explain the properties of Laplace transforms in Detail.	7
b)	A series RLC circuit has a resistance of 20Ω , a capacitance of $0.02\mu\text{F}$, and an inductance of 0.02H . Find the resonance frequency and half power frequencies.	7
7. a)	Derive the relationship between impedance and admittance parameters.	6
b)	<p>Determine the transmission parameters of the network shown in below figure.</p> 	8
8. a)	Explain the convolution Integral in detail.	6
b)	<p>Determine the Admittance(Y) parameters for the following network.</p> 	8