



ACE Engineering College

(An Autonomous Institution)

Question Paper Code:

EE401ES

ACE-R20

Semester End Examination II B. Tech- II Semester- AUGUST -2022 Principles of Electrical and Electronics Engineering

Common to CE, MECH

Time: 3 Hours

Max. Marks: 70

H. T. No

Answer any 5 Questions out of 8 Questions from the following

| Q.No | Question | Marks |
|-------|--|-------|
| 1. a) | Explain star to delta conversion in a DC circuit. | 7 |
| b) | Three resistors: $R_1=5\Omega$, $R_2=10\Omega$, $R_3=15\Omega$ are connected in parallel across a DC voltage source: 100V. Determine the currents I_1 , I_2 , I_3 through R_1 , R_2 , R_3 and the total current supplied by 100V source. | 7 |
| 2. a) | With neat diagram explain the construction and working of transformer | 7 |
| b) | Derive the Torque equation of DC Motor | 7 |
| 3. a) | Explain lead acid cell battery with neat diagram | 7 |
| b) | Write short note on (i) MCB (ii) MCCB | 7 |
| 4. a) | Describe the different speed control techniques available for DC shunt motor | 7 |
| b) | Explain the different types of three phase transformer connection | 7 |
| 5. a) | State and Explain Ohms Law, Kirchoff's Voltage Law and Kirchoff's Current Law | 7 |
| b) | Derive the expression for RMS value of an AC voltage Waveform. | 7 |
| 6. a) | How Zener diode is used as a voltage regulator? Explain | 7 |
| b) | Explain the significance of filters in Rectifiers and explain different types of filters? | 7 |
| 7. a) | Draw the schematic diagram of P-Channel JFET. Explain the drain and transfer characteristics | 7 |
| b) | The P-channel FET has a $ I_{DSS} =-12\text{mA}$, $ V_p =5\text{V}$, V_{GS} is 1.6 V. Determine I_D and G_m | 7 |
| 8. a) | Draw the input, output characteristics of a Common Emitter configuration, and explain in detail. | 7 |
| b) | In a common emitter configuration, if $I_E = 5\text{mA}$, $I_B = 10 \mu\text{A}$ then find the values of α , β , γ . | 7 |