## AG AG AG AG AG AG AG A

AG	de No: 156CK  JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD  B. Tech III Year II Semester Examinations, August - 2022  POWER SYSTEM OPERATION AND CONTROL  (Electrical and Electronics Engineering)  Answer any five questions  All questions carry equal marks	F
△(1.a) b)	Explain the procedure for formation of nodal admittance matrix by step by step procedure.  Form the $Y_{BUS}$ for the network shown in figure, including the generator buses 1 and 2 with impedance of 0.1, 0.4 p.u. respectively. All the values are p.u. impedances for the network.  [7+8]	/
AC	AG A	1
	Explain about the classification of buses with neat/sketch.  Explain Gauss-Seidel iterative method for power flow analysis of any power system with a flow chart.  [6+9]	_
3.a) b)	Derive generalized expression for transmission loss in a n-bus network.  150 MW, 220 MW and 220 MW are the ratings of three units located in a thermal power station. Their respective incremental costs are given by the following equations: $\frac{dC_1}{dP_1} = Rs(0.11P_1 + 12)$ $\frac{dC_2}{dP_2} = Rs(0.095P_2 + 14)$ $\frac{dC_3}{dP_3} = Rs(0.1P_3 + 13)$	
AG	Where P <sub>1</sub> , P <sub>2</sub> and P <sub>3</sub> are the loads in MW. Determine the economical load allocation between the three units, when the total load on the station is (i) 350 MW (ii) 500 MW.  [6+9]	<u> </u>
4.a) b)	Define penalty factor and state its significance.  Derive relevant equations to explain economic dispatch of thermal plants coordinating the system transmission losses.  [7+8]	
AG	AG AG AG AG AG AG	<u>/\</u>

## AG AG AG AG AG AG A

